
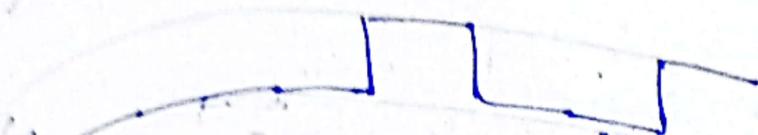


Question # 01

FROM TRUTH TABLE:

S0	S1	C0
0	0	0
1	0	0
0	1	0
0	1	0
0	0	1
1	1	0
1	1	0
1	1	1

Waveforms

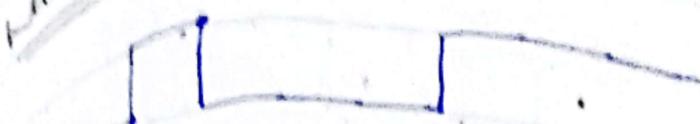

X

X

Question # 02 :-


A1	A0	B1	B0	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

Waveform :-

A > B :-



A = B :-

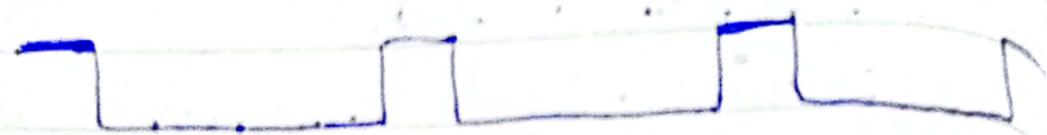


A < B :-




X ————— X

Question # 03 :-


(a) 1101

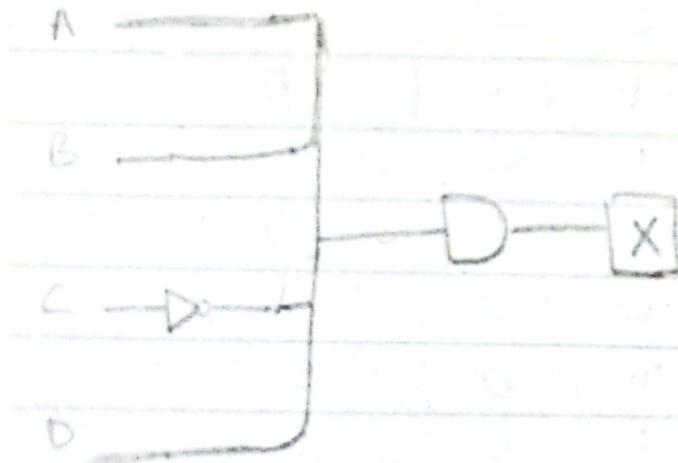


(b) 1000

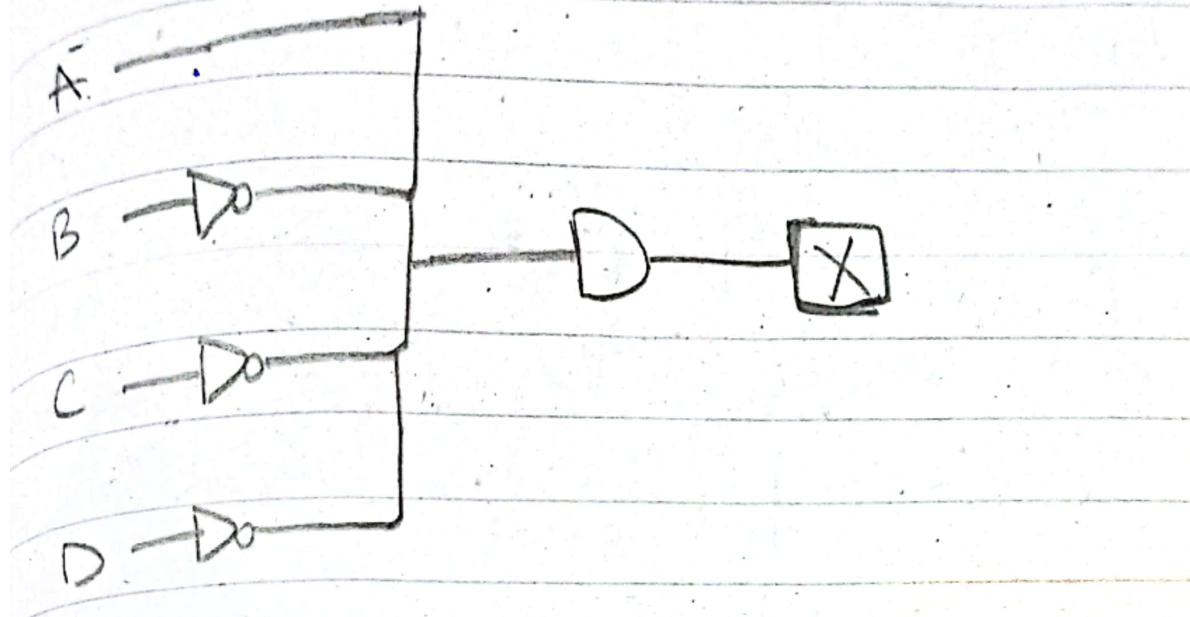

(c) 11011

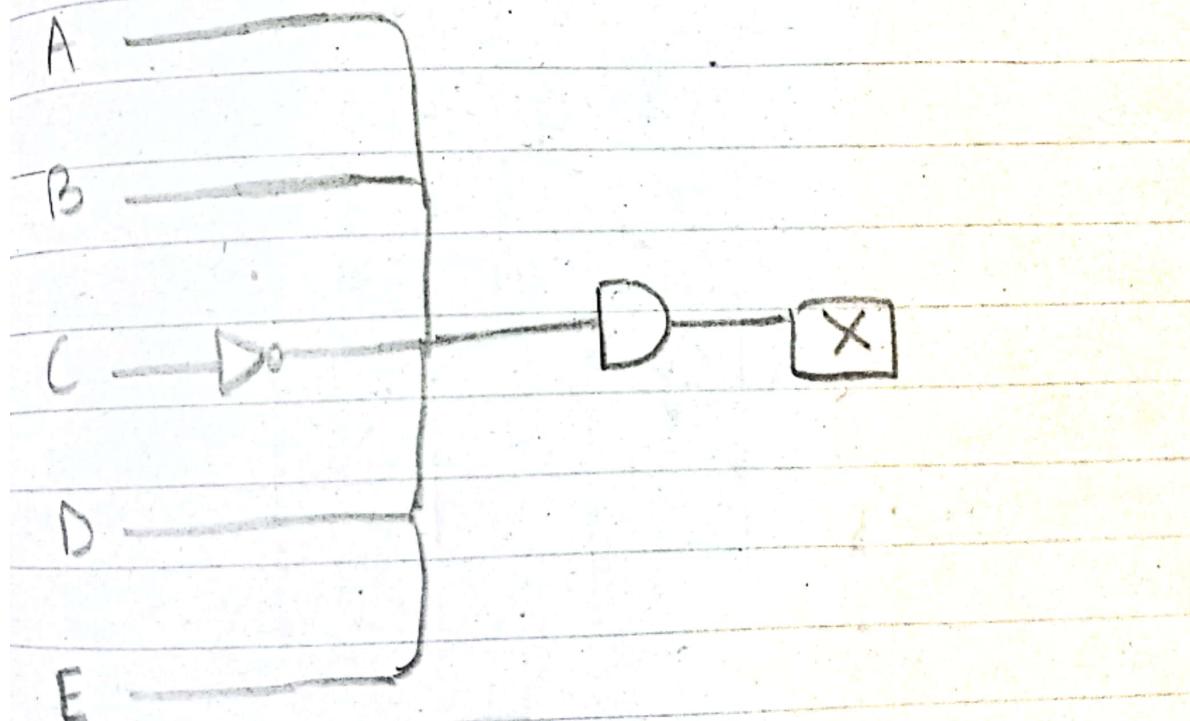

(d) 11100

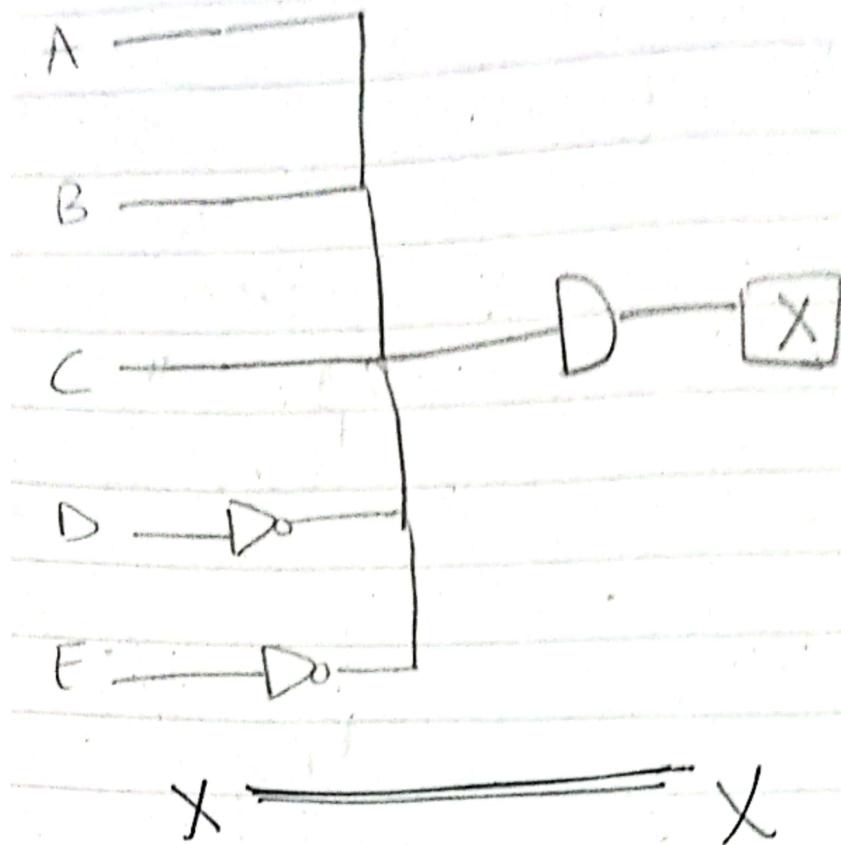

Question # 04 :-

AB\CD	00	01	11	10	01	11	10
00		1					
01							
11	1						
10				1	1	D	

$$\text{Eqn: } \overline{A}\overline{B}\overline{C}D + A\overline{B}\overline{C}D + ABC$$

Question # 05:

Eqn:-

$$\bar{A}_0 A_1 A_2 + A_0 \bar{A}_1 A_2 + \bar{A}_0 A_1 \bar{A}_2$$

Truth Table:

A_2	A_1	A_0	\bar{A}_2	\bar{A}_1	\bar{A}_0	$\bar{A}_0 A_1 A_2$	$A_0 \bar{A}_1 A_2$	$\bar{A}_0 A_1 \bar{A}_2$	F
0	0	0	1	1	1	0	0	0	0
0	0	1	1	1	0	0	0	0	0
0	1	0	1	0	1	0	0	1	1
0	1	1	1	0	0	0	0	0	0
1	0	0	0	1	1	0	0	0	0
1	0	1	0	1	0	0	1	0	1
1	1	0	0	0	1	1	0	0	1
1	1	1	0	0	0	0	0	0	0

Output Waveform:

F

1 2 3 4 5

Question # 06:-

- 0) 1000 → 8
- 1) 0100 → 4
- 2) 0010 → 2
- 3) 0110 → 6
- 4) 1001 → 9
- 5) 0100 → 4
- 6) 0010 → 2
- 7) 0110 → 6
- 8) 0001 → 1

0.

1.

2.

3.

4.

5.

6.

7.

8.

9.


Question 1 + 07

If 9 and 3 are high, then according to the logic of the circuit the answer should be 12 in binary ~~1010~~
i.e. ~~1010~~ but we get ~~1010~~
1011 i.e. the binary of 11.

So, the BCD representation of 11
is invalid.

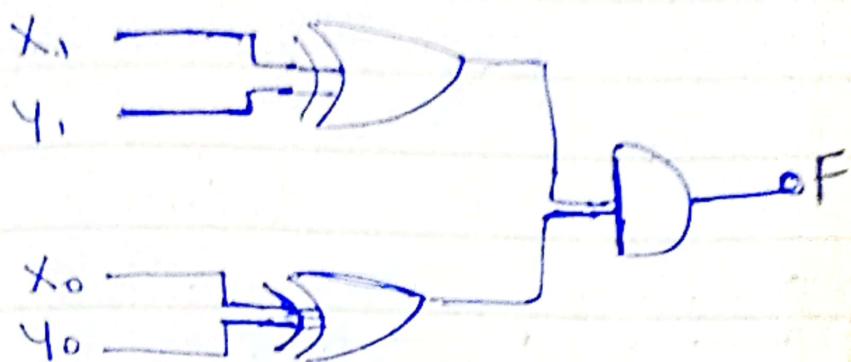Question # 08

We need to design a circuit when the corresponding bits are opposite to each other so we will get an XOR gate because it gives high output on 2 opposite inputs.



$$F = (X_1 \oplus Y_1) \cdot (X_0 \oplus Y_0)$$

Question # 09

Truth Table:-

A	B	Diff	Carry
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Diff :-

A	B	0	1
0	0	1	
1	1	0	


Carry :-

A	B	0	1
0	0	1	
1	0	0	


$$D = (\bar{A}B + A\bar{B})$$

$$C = \bar{A}B$$

- Logic circuit using XOR & AND.

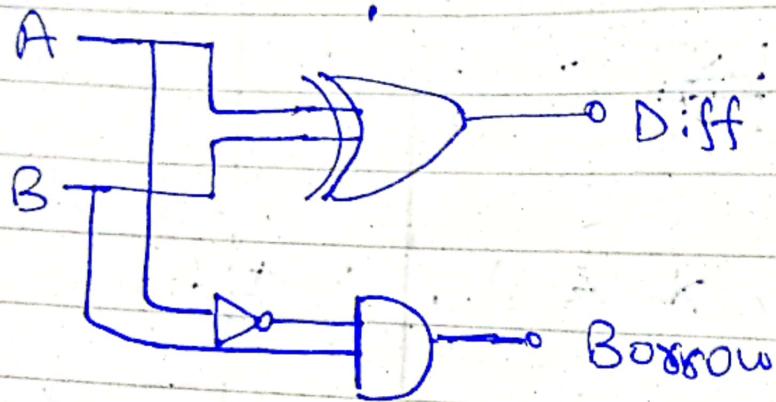

- Using NOR gate:-

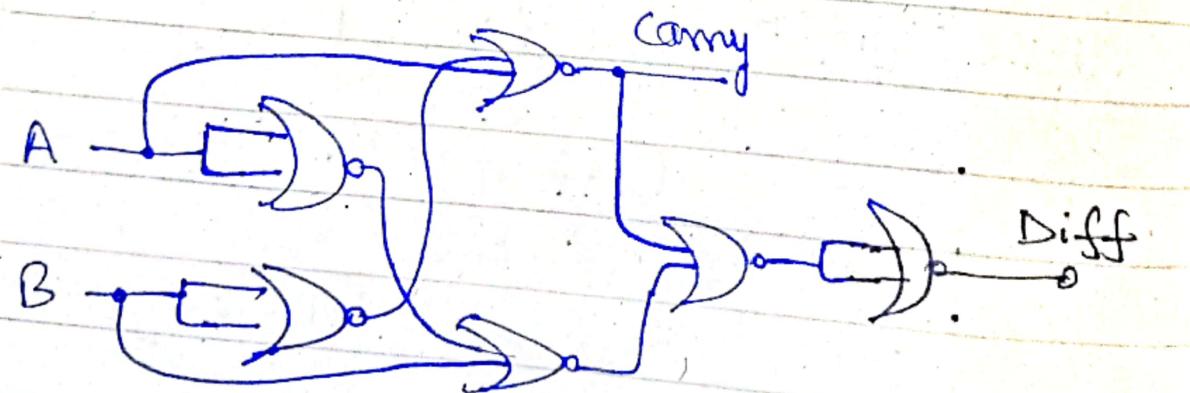

(Q) Truth Table

A_2	A_1	B_2	B_1	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

• For $A > B \doteq A_1\bar{B}_2\bar{B}_1 + A_2\bar{B}_2 + A_2A_1$

A_2A_1	B_2B_1	00	01	11	10	1
00						
01		1				
11		1	1		1	
10		1	1			

• For $A = B \doteq (A_1 \oplus B_1)(A_2 \oplus B_2)$

A_2A_1	B_2B_1	00	01	11	10	1
00		1				
01			1			
11				1		
10					1	

• For $A < B \doteq \bar{A}_2\bar{A}_1B_1 + A_2B_2 + \bar{A}_1B_2B_1$

A_2A_1	B_2B_1	00	01	11	10	1
00		1	1	1		
01			1	1		
11						
10			1			

(11) Sol:

(a) $S_0 = 0, S_1 = 1 \Rightarrow S = 10 = 2$

$$Y = D_2$$

$$\boxed{Y = 0}$$

$$\therefore D_2 = 0$$

(b) $S_0 = 1, S_1 = 1 \Rightarrow S_1 = 11 \Rightarrow 3$

$$Y = D_3$$

$$\boxed{Y = 1}$$

$$\therefore D_3 = 1$$


(c) $S_0 = 1, S_1 = 0 \Rightarrow S = 1$

$$Y = D_1$$

$$\boxed{Y = 0}$$

$$\therefore D_1 = 0$$

(12)

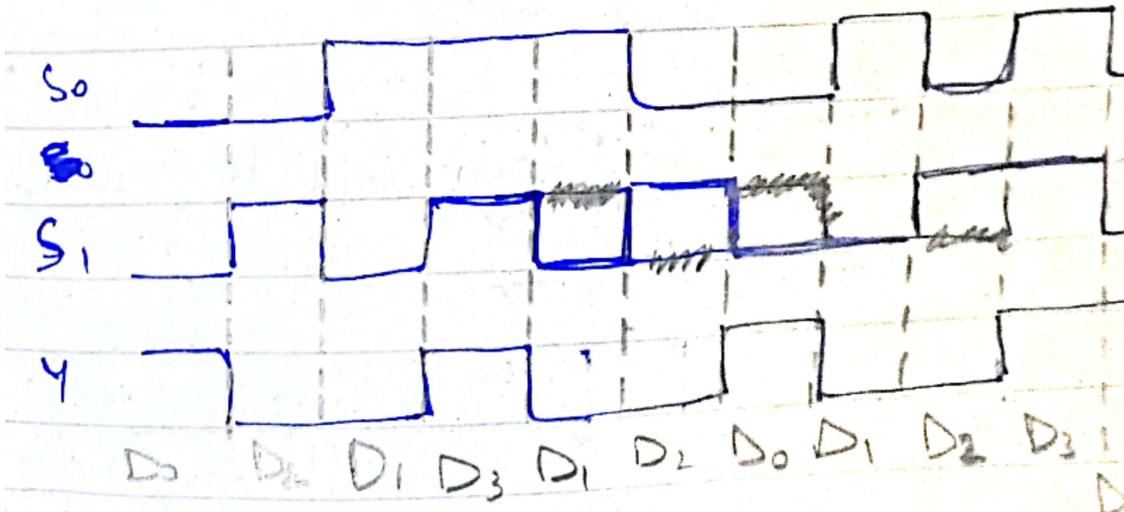


(B)


E	E	S ₂	S ₁	S ₀	Y
0	0	0	0	0	I ₀
1	0	0	0	1	I ₁
1	0	0	1	0	I ₂
1	0	0	1	1	I ₃
1	1	0	0	0	I ₄
1	1	0	0	1	I ₅
1	1	1	0	0	I ₆
1	1	1	1	1	I ₇

Output Waveform:


With E :-

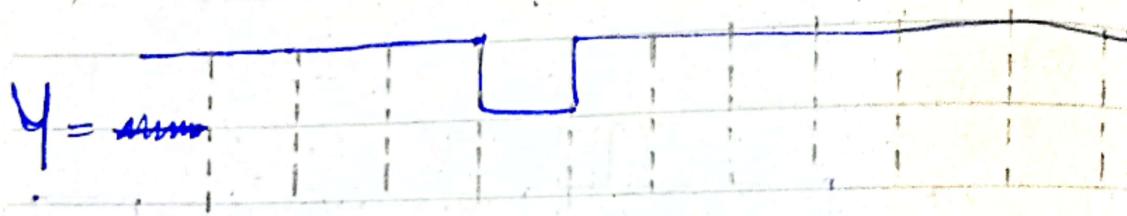

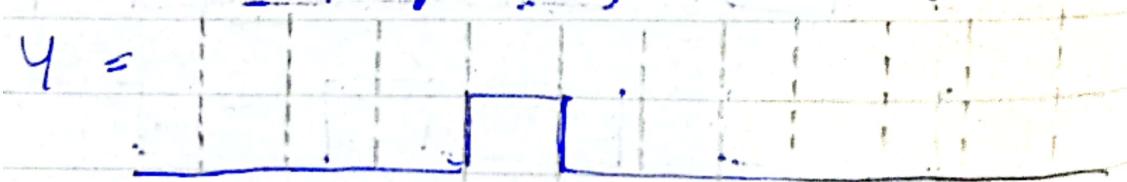With \bar{E} , the wave form will be inverse




(14)

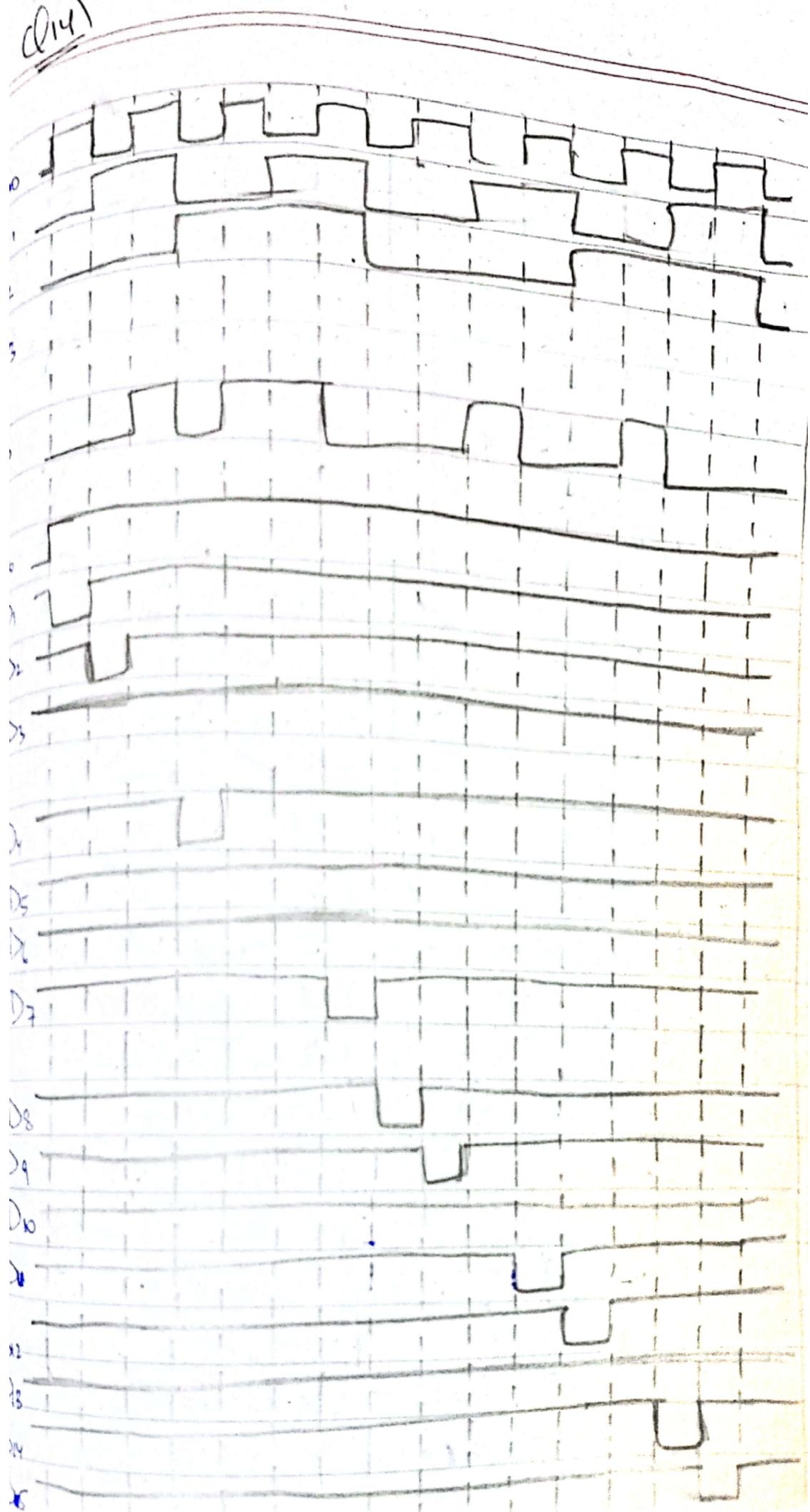

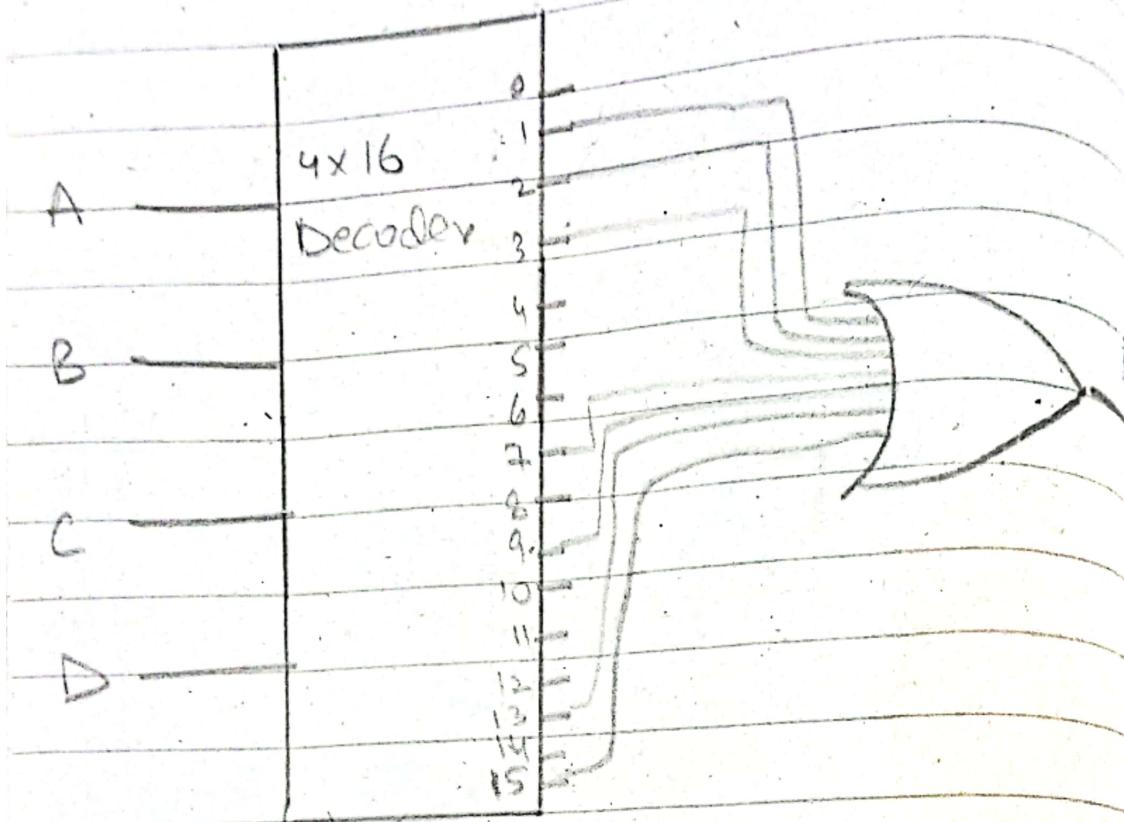Q15 Given eqn/function:

$$F(A, B, C, D) = \Sigma (1, 2, 3, 7, 9, 13, 15)$$




Q16 X(A₃, A₂, A₁, A₀) = Σ (2, 3, 4, 8, 9, 10, 11, 15)

A₃A₂ \ A₁A₀

	00	01	11	10
00			1	1
01	1			
11			1	
10	1	1	1	1
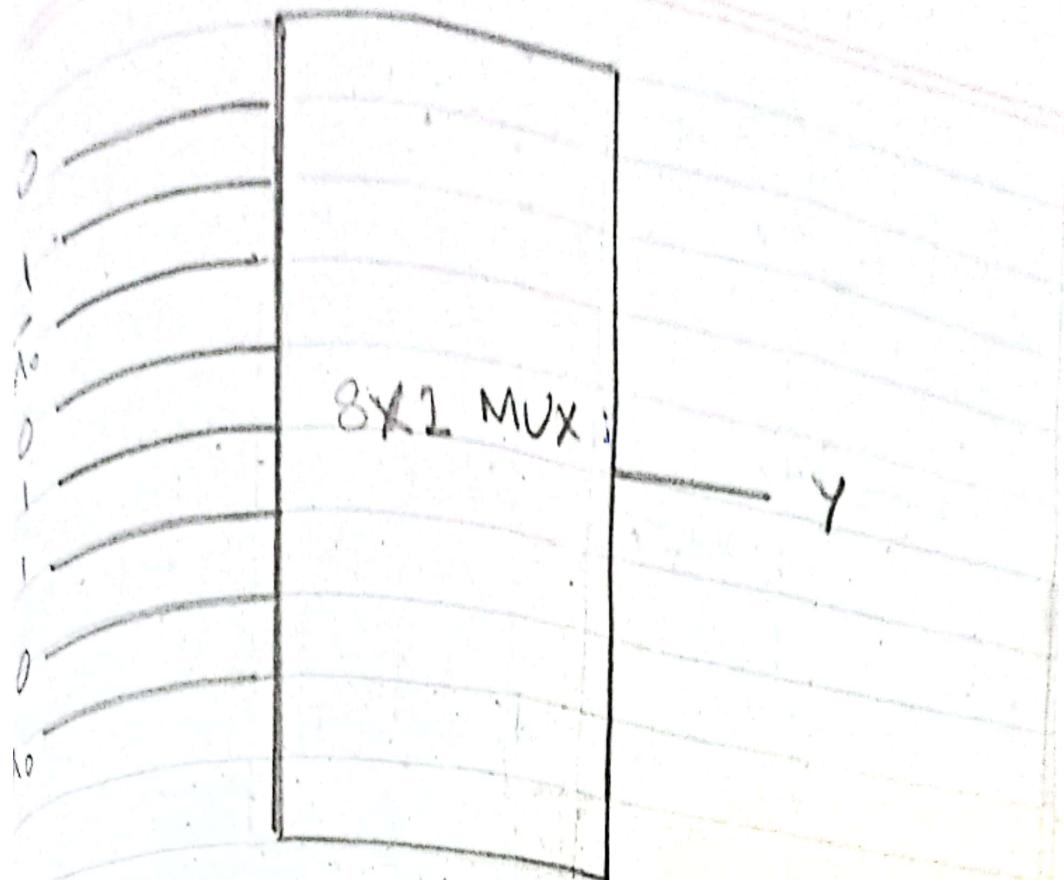
$$\begin{aligned} Fx &= \bar{A}_2 A_1 + A_3 \bar{A}_2 + \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0 \\ &\quad + A_3 A_1 A_0 \end{aligned}$$



$$\begin{aligned}
 &= \bar{A}_3 \bar{A}_2 A_1 + \bar{A}_3 A_2 \bar{A}_1 A_0 + A_3 \bar{A}_2 \bar{A}_1 + A_3 \bar{A}_2 A_1 \\
 &\quad + A_3 A_2 A_1 A_0
 \end{aligned}$$

$$\begin{aligned}
 &= \bar{A}_3 \bar{A}_2 A_1 + A_3 \bar{A}_2 A_1 + \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0 + A_3 \bar{A}_2 \bar{A}_1 \\
 &\quad + A_3 A_2 A_1 A_0
 \end{aligned}$$

$$\begin{aligned}
 &= \bar{A}_2 A_1 (A_3 + \bar{A}_3) + \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0 + A_3 \bar{A}_2 \bar{A}_1 + A_3 A_2 A_1 A_0
 \end{aligned}$$

$$\begin{aligned}
 &= \bar{A}_2 A_1 + \bar{A}_3 \bar{A}_2 \bar{A}_1 + \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0 + A_3 A_2 A_1 A_0
 \end{aligned}$$

$$\begin{aligned}
 &= \bar{A}_2 (A_1 + \bar{A}_3) + \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0 + A_3 \bar{A}_2 A_1 A_0
 \end{aligned}$$


$$\begin{aligned}
 &= \bar{A}_2 (A_1 + A_3) + A_3 A_2 \bar{A}_1 \bar{A}_0 + A_3 A_2 A_1 A_0
 \end{aligned}$$

$$= A_3 \bar{A}_2 + \bar{A}_2 A_1 + \bar{A}_3 A_2 \bar{A}_1 A_0 + A_3 A_2 A_1 A_0$$

$$= A_3 \bar{A}_2 + A_3 A_2 A_1 A_0 + \bar{A}_2 A_1 + \bar{A}_3 A_2 A_1 A_0$$

$$\cancel{= A_3} \rightarrow = X$$

QF) (a)

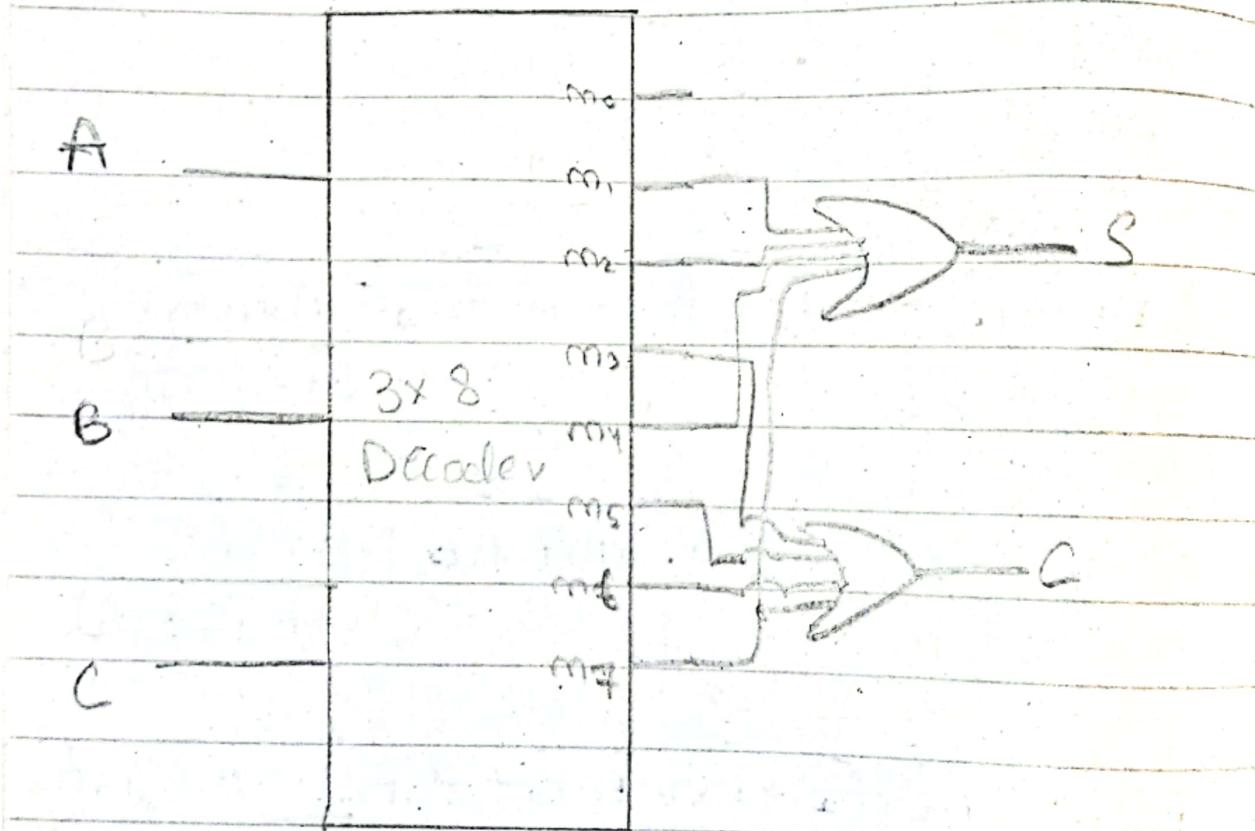

A	B	Cin	S	C	
0	0	0	0	0	
0	0	1	1	0	m_0
0	1	0	1	0	m_1
0	1	1	0	1	m_2
1	0	0	1	0	m_3
1	0	1	0	1	m_4
1	1	0	0	1	m_5
1	1	1	1	1	m_6
					m_7

$$S = \Sigma (m_1, m_2, m_4, m_7)$$

$$C = \Sigma (m_3, m_5, m_6, m_7)$$



Question # 14 (b) :

For S :-

A	BCin	00	01	11	10
0		1	1		1
1		1	1	1	

For C :-

A	BCin	00	01	11	10
0		1		1	
1		1	1	1	1

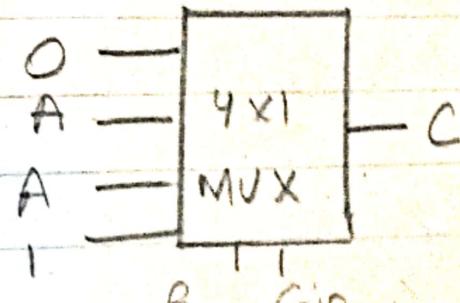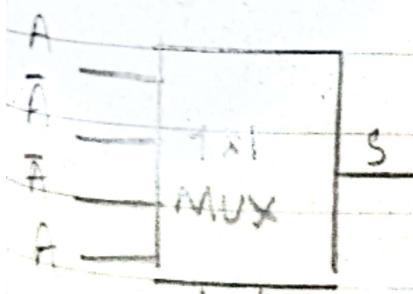

(Q8)

