


## Lab Tasks

### Lab Task#1:

- Design one-bit comparator Circuit on the Logic Works and develop truth table of it.
- Design two-bit comparator Circuit on the Logic Works and develop truth table of it.


**Lab Task#2:** Apply each of the following sets of binary numbers to the comparator inputs in the following Figure, and determine the output by following the logic levels through the circuit.

- 10 and 10
- 11 and 10

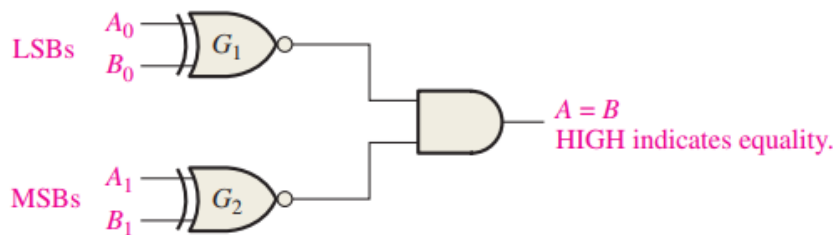

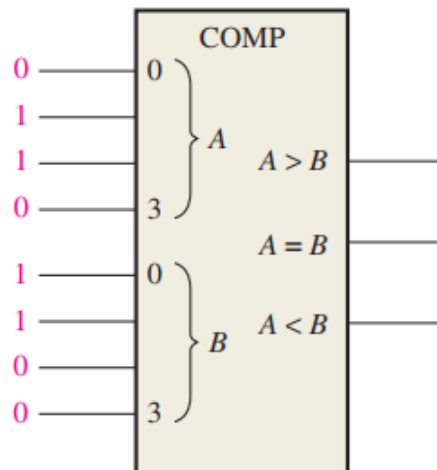**Implement on the Logic Works as well**

**Lab Task#3:** Implement on the Logic Works using 74HC85, and determine the  $A = B$ ,  $A > B$ , and  $A < B$  outputs for the input numbers shown on the comparator in the following Figure:



**Lab Task#4:** Use 74HC85 comparators to compare the magnitudes of two 8-bit numbers. Show the comparators with proper interconnections.

